



Module 8

Lecture : Interfacing input and output - Switches

2




Interfacing input devices using Switches

You will learn in this module

- Fundamentals of switches
- How to interface switches TI's Launchpad Development board
- Software driver (set of functions to create an abstract module)
- Motivation for lab

Relevance: Bumper Switches

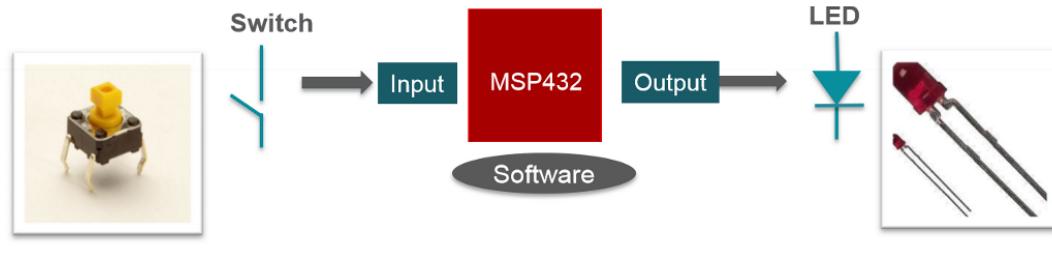- Translate the robot hitting an object into software and handle that issue



3


| Interfacing input and output - Switches

Texas Instruments Robotics System Learning Kit: The Solderless Maze Edition
SEKP100



Switch Configuration


2 States
Not pressed Pressed

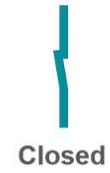


Not pressed $R = 100\text{M}\Omega$
Pressed $R = 0.1\Omega$

Reality

Reality

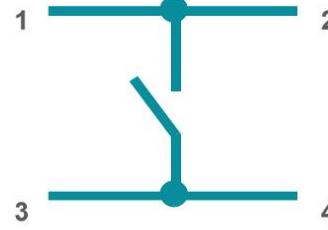

1 switch,
4 wires

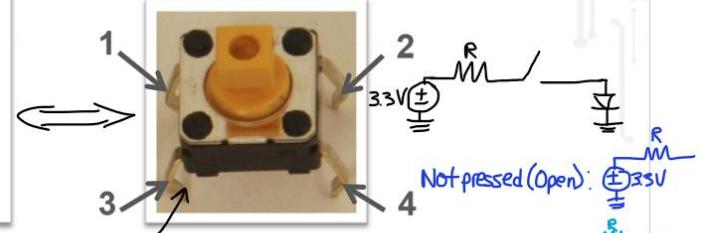


Not pressed (Open): $\text{±}3.3\text{V}$
Pressed (Closed): $\text{±}3.3\text{V}$

Texas Instruments Robotics System Learning Kit: The Solderbots™ Micro Edition



Positive Logic Switch Interface (2 ways to use it)

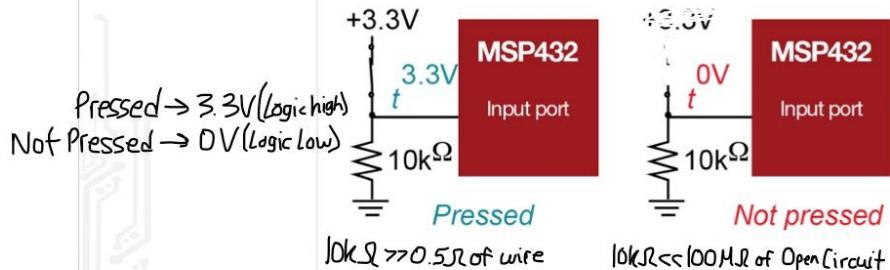Pull-Down Resistor \Leftrightarrow Positive Logic




Positive Logic t
- pressed, 3.3V, true
- not pressed, 0V, false



Negative Logic Switch Interface

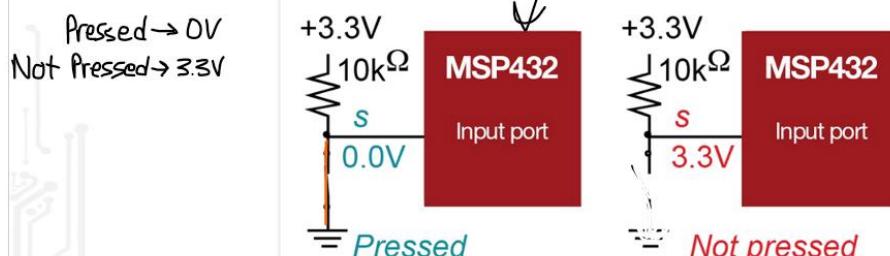Pull-Up Resistor \Leftrightarrow Negative Logic




Negative Logic s
- pressed, 0V, true
- not pressed, 3.3V, false

No advantages between
 (\rightarrow) vs (\leftarrow) logic



LaunchPad Switches and LEDs

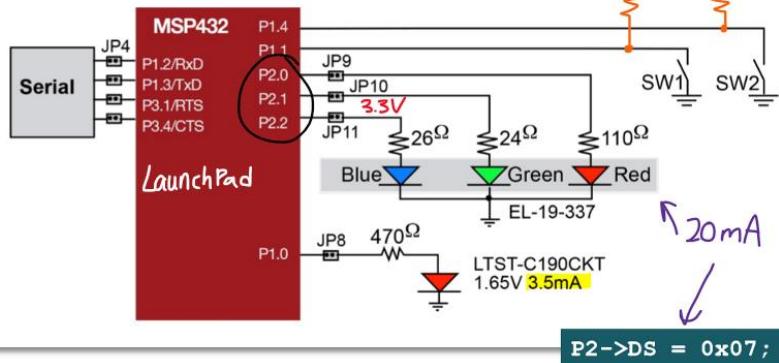

The Switches on the LaunchPad

- Negative logic
- Require internal pull-up

The LEDs are positive logic

7

| Interfacing input and output - Switches

Texas Instruments Robotics System Learning Kit: The Solderless Maze Edition
SEKP100

Software Driver (inputs)

↳ functions that let you use a device (here, the switches)

Initialization (executed once at beginning)


1. Set DIR to 0 for input
2. Enable pullup on inputs

All here works for
Positive and Negative
Logic

Mask

Input from switches

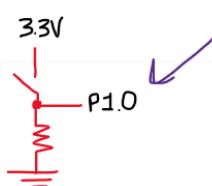1. Read from data input port
2. Mask (select) desired bits



`P1->IN → 7 6 5 4 3 2 1 0
&
0 0 0 0 0 0 0 1
—————
0 0 0 0 0 0 ?`

Extract only the bit
that we want

For Positive Logic
?=1 if pin is pressed
?=0 if pin is not pressed

8

| Interfacing input and output - Switches

Texas Instruments Robotics System Learning Kit: The Solderless Maze Edition
SEKP100



Software Driver (simple, **not friendly**)

```
#include "msp.h" // initializes both the switches shown earlier
void Port1_Init(void){
    P1->DIR = 0x00; // 1) make P1.4 and P1.1 in
    P1->REN = 0x12; // 2) enable pull resistors on P1.4 P1.1
    P1->OUT = 0x12; // P1.4 and P1.1 are pull-up
}
uint8_t Port1_Input(void){
    return (P1->IN&0x12); // read P1.4,P1.1 inputs
}
```

7654 3210
0000 0000
★ ★
P1->REN = 0x12
= 0001 0010
7654 3210 ★

See [InputOutput_MSP432](#) example project



Software Driver (friendly)

Initialize
Switches
Read the
switches

```
#include "msp.h"
void Port1_Init(void){
    P1->DIR &= ~0x12; // 1) make P1.4 and P1.1 in
    P1->REN |= 0x12; // 2) enable pull resistors on P1.4 P1.1
    P1->OUT |= 0x12; // P1.4 and P1.1 are pull-up
}
uint8_t Port1_Input(void){
    return (P1->IN&0x12); // read P1.4,P1.1 inputs
}
```

See [InputOutput_MSP432](#) example project


Pullup
REN=1
Out=1 for respective bits
DIR=0



Application

Switches provide

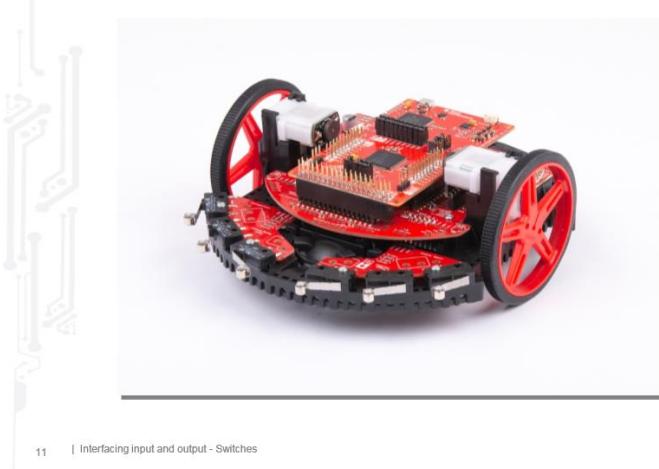1. Feedback to robot as bump sensors to determine if there is an obstruction
2. Control/command inputs to robot (e.g., start/stop)



11 | Interfacing input and output - Switches



Texas Instruments Robotics System Learning Kit: The Solderless Maze Edition
SEKP100


Voltage = Current x Resistance



Summary

- Positive and negative logic
- Ohm's Law for resistors
- Switch interface with pullup or pulldown
- LaunchPad switches and LEDs
- Software driver
 - Initialization
 - Input/Output functions

$$V = I * R$$

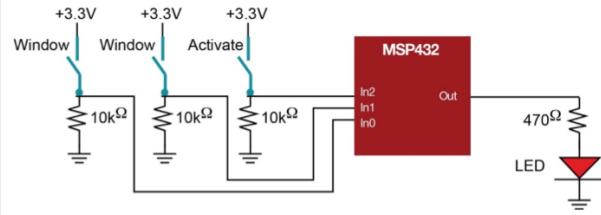

12 | Interfacing input and output - Switches

Texas Instruments Robotics System Learning Kit: The Solderless Maze Edition
SEKP100